

EE/EET 2240
Homework Problem #16

Use mesh analysis followed by Ohm's Law to determine V_x in the circuit shown below.

