

EE 2240

**Homework Problem #19**

$X$  and  $Y$  are linear components. If  $I_0 = 20$  mA when  $V_S = 125$  V, what will be the new value of  $I_0$  if  $V_S$  is increased to 200 V?

