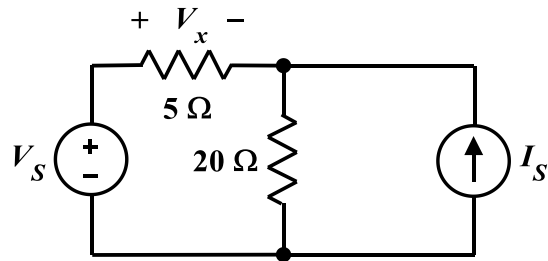


EE 2240
Homework Problem #20



V_x can be described by the equation

$$V_x = K_1 I_S + K_2 V_S$$

Determine K_1 and K_2 .