

EE/EET 2240
Homework Problem #20

Use mesh analysis to find V_o in the circuit shown.

