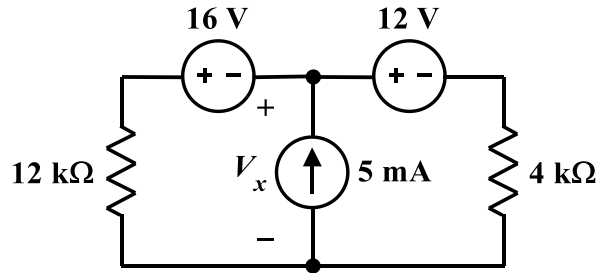


EE/EET 2240  
**Homework Problem #24**



Use the superposition method to determine the value of  $V_x$ .