
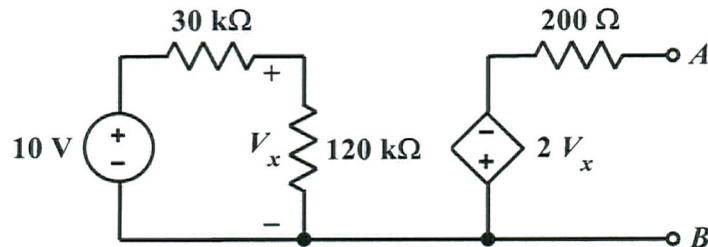


Homework Problem #32

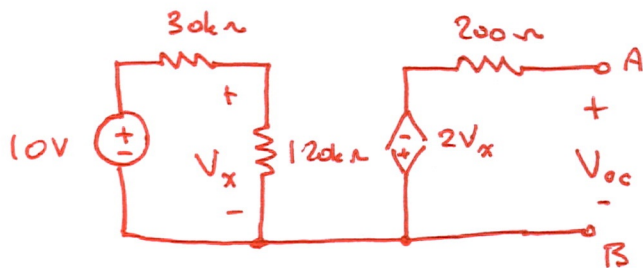


Find the Norton equivalent circuit with respect to terminals A and B .



$$V_x = \frac{120 \text{ k}\Omega}{150 \text{ k}\Omega} \cdot 10 \text{ V} = 8 \text{ V}$$

$$V_{oc} = -2V_x = -16 \text{ V}$$

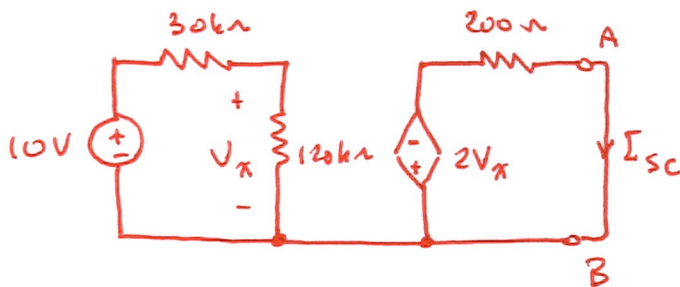

$$V_x = \frac{120 \text{ k}\Omega}{150 \text{ k}\Omega} \cdot 10 \text{ V} = 8 \text{ V}$$

$$I_{sc} = -\frac{2V_x}{200 \Omega} = -0.08 \text{ A}$$

$$\therefore I_N = I_{sc} = -0.08 \text{ A}$$

$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{-16 \text{ V}}{-0.08 \text{ A}} = 200 \Omega$$

The Norton equivalent circuit is:

