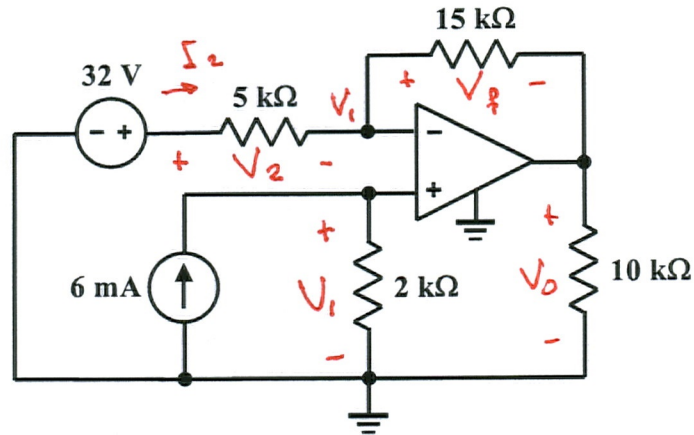


EE/EET 2240  
Homework Problem #35



The OpAmp is ideal. Determine the amount of power absorbed by the 10 kΩ resistor.

$$V_1 = (2\text{ k}\Omega)(6\text{ mA}) = 12\text{ V}$$

$$V_2 = 32\text{ V} - V_1 = 32\text{ V} - 12\text{ V} = 20\text{ V}$$

$$I_2 = \frac{V_2}{5\text{ k}\Omega} = 4\text{ mA}$$

$$V_f = (15\text{ k}\Omega)(I_2) = 60\text{ V}$$

$$V_o = -V_f + V_1 = -48\text{ V}$$

$$P_{10\text{ k}\Omega} = \frac{V_o^2}{10\text{ k}\Omega} = \frac{(-48\text{ V})^2}{10\text{ k}\Omega} = 230.4\text{ mW}$$