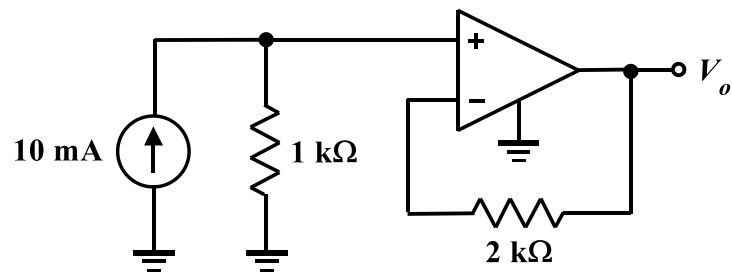


EE 2240
Homework Problem #38



The OpAmp is ideal. Determine the value of V_o .