
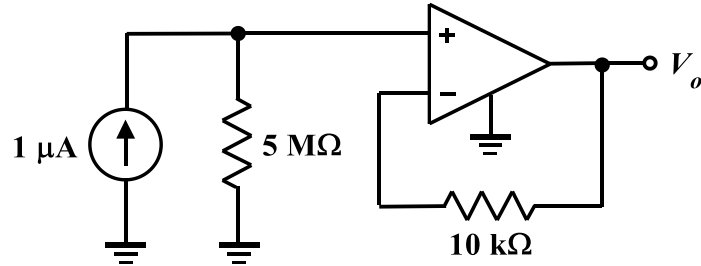


EE/EET 2240
Homework Problem #39

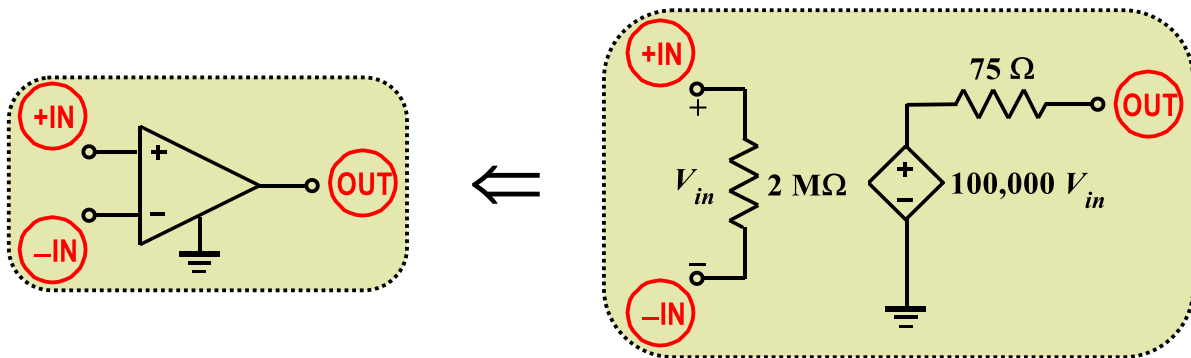

Use Pspice to determine the value of V_o . Use the model shown below for the OpAmp.



Submit a complete printed copy of your output file, and highlight the answer in some obvious manner. (Don't forget to put a personal identifier in the title line of your input circuit description file (also called the netlist).