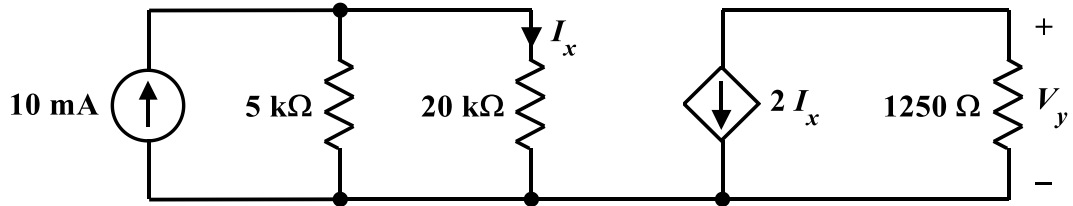


EE 2240  
**Homework Problem #43**



Use PSpice to determine the values of  $I_x$  and  $V_y$ . Submit a complete printed copy of your output file, and highlight the answers in some obvious manner. (Don't forget to put a personal identifier in the title line of your input circuit description file (also called the netlist).