

$$-V_x + V_y = 0$$

$$\Rightarrow V_y = V_x = 10V$$

PSC

\Rightarrow absorbing

$$P = (10V)(2A)$$


$$= 20W$$

~~PSC~~

\Rightarrow delivering

$$P = (10V)(2A)$$


$$= 20W$$

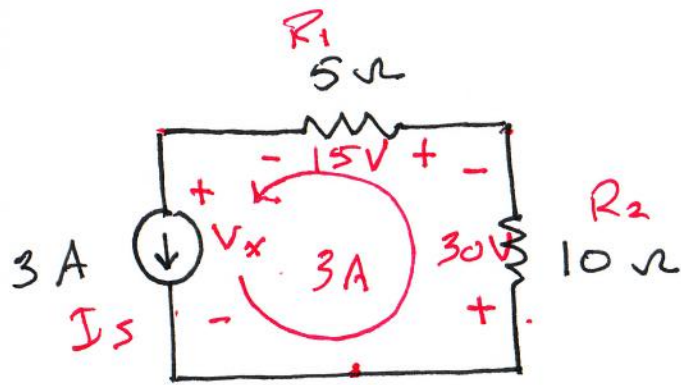

R_1 absorbs $(3A)(15V) = 45W$
 R_2 absorbs $(3A)(30V) = 90W$
 I_s delivers $(3A)(45V) = 135W$

$$-V_x - 15V - 30V = 0$$

$$\Rightarrow V_x = -45V$$

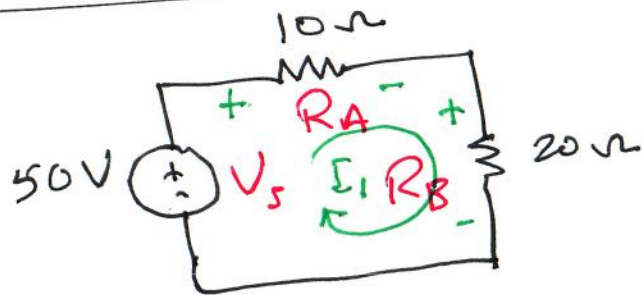

R_A absorbs $(10\Omega)(\frac{5}{3}A)(\frac{5}{3}A) = \frac{250}{9}W$
 R_B absorbs $(20\Omega)(\frac{5}{3}A)(\frac{5}{3}A) = \frac{500}{9}W$
 V_s delivers $(50V)(\frac{5}{3}) = \frac{250}{3}W$

$$\text{KVL: } R_A I_1 + R_B I_1 - 50V = 0$$

$$10 I_1 + 20 I_1 = 50V$$

$$30 I_1 = 50$$

$$I_1 = \frac{5}{3} A$$

$$P = VI$$

\uparrow \uparrow

$R I$ $\frac{1}{R} V$

$$= R I^2$$
$$= \frac{1}{R} V^2$$


short cuts

KVL

KCL

Ohm's Law

$$P = VI$$

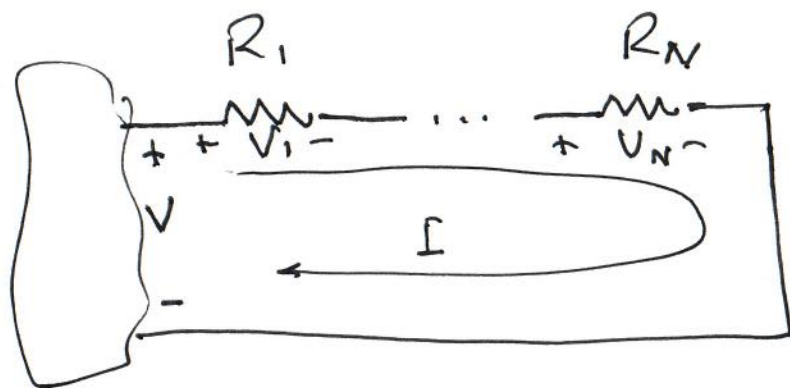

Resistors in series

$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$\vdots$$

$$V_N = R_N I$$

$$V = V_1 + V_2 + \dots + V_N \quad (\text{KVL})$$

$$= R_1 I + R_2 I + \dots + R_N I$$

$$V = \underbrace{(R_1 + R_2 + \dots + R_N)}_{R_{eq}} I$$

$$V = R_{eq} I$$

where



$$R_{eq} = R_1 + \dots + R_N$$

for series resistors

$$V_k = R_k I$$

$$\frac{V_k}{V} = \frac{R_k I}{R_1 I + R_2 I + \dots + R_N I}$$
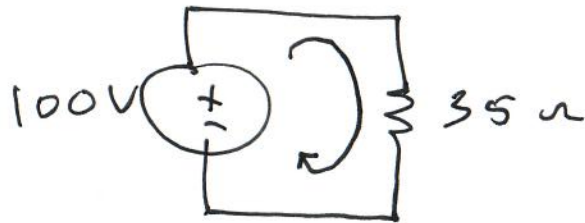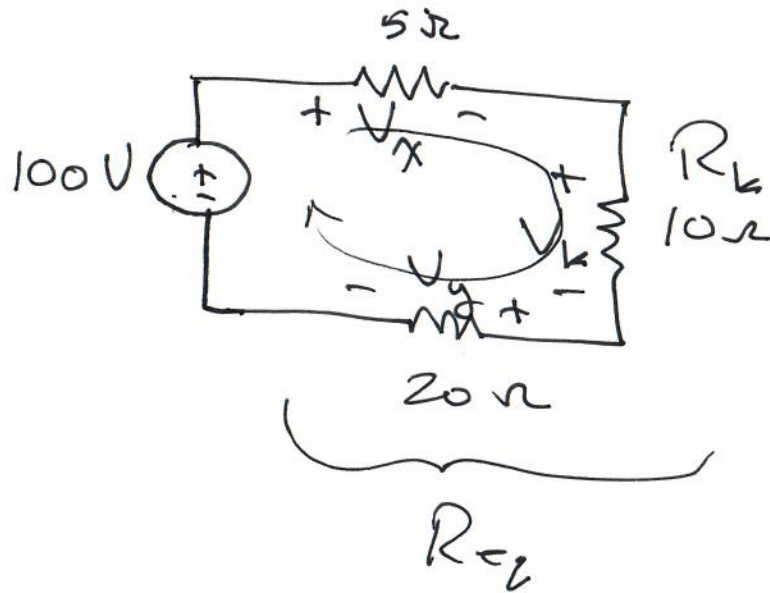
$$\frac{V_k}{V} = \frac{R_k}{R_1 + \dots + R_N} \quad \text{Voltage Divider}$$




$$\frac{V_k}{100V} = \frac{10}{5 + 10 + 20} = \frac{10}{35}$$


$$V_k = \frac{10}{35} \cdot 100V = \frac{1000}{35} V = \frac{200}{7} V$$

$$\frac{V_x}{100V} = \frac{5}{5 + 10 + 20} = \frac{5}{35}$$
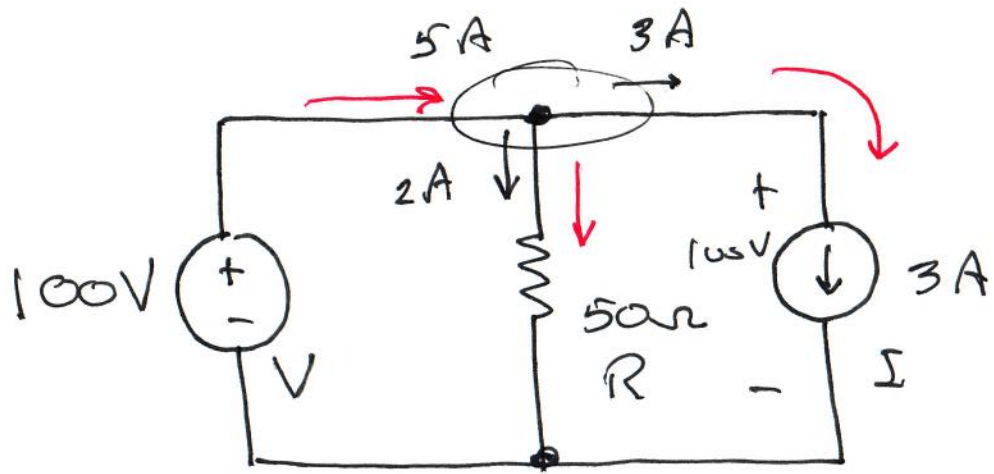
$$V_x = \frac{500}{35} = \frac{100}{7} V$$



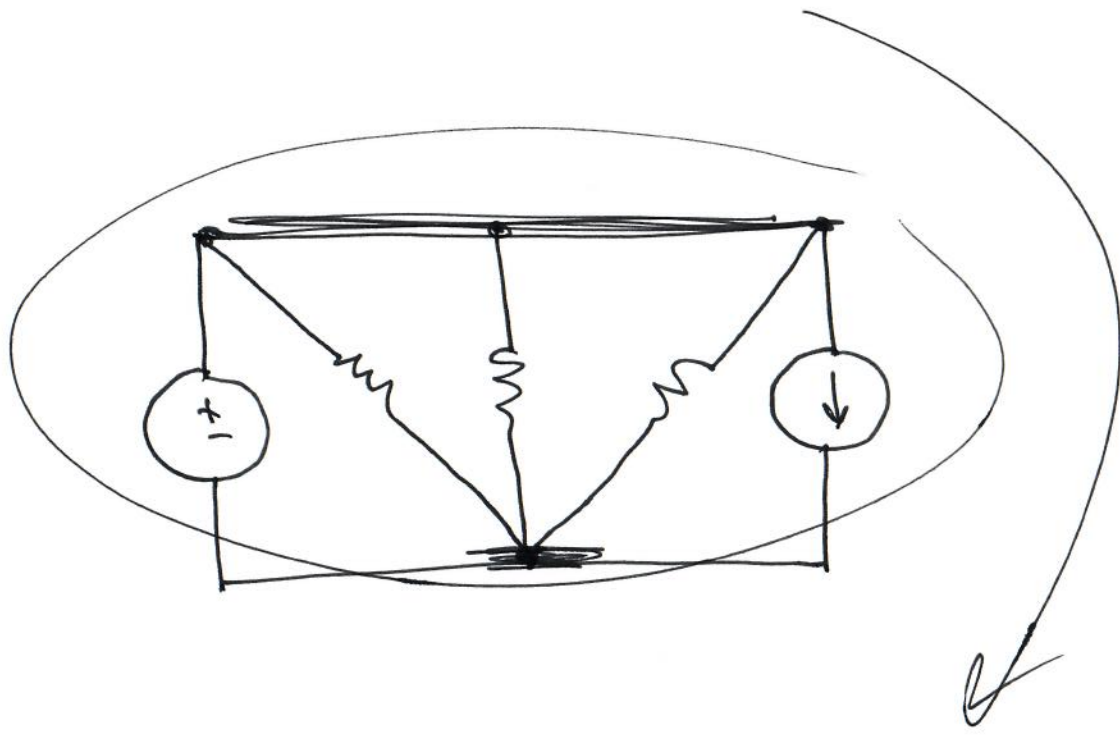parallel
connection
 \Rightarrow same
voltage



$$\begin{array}{l} R \text{ absorbs } \frac{(100V)^2}{50\Omega} = 200W \\ I \text{ absorbs } (100V)(5A) = 300W \\ V \text{ delivers } (100V)(5A) = 500W \end{array} \left. \vphantom{\begin{array}{l} R \\ I \\ V \end{array}} \right\} \begin{array}{l} 500W \\ \text{absorbed} \end{array}$$