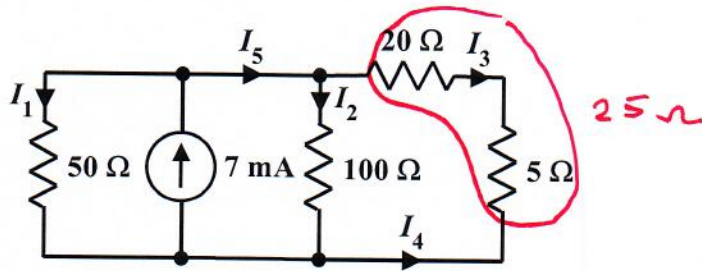


EE/EET 2240
Homework Problem #009



a. Use the current divider equation to determine I_1 .

b. Use the current divider equation to determine I_2 .


c. Use the current divider equation to determine I_3 .

$$I_3 = \frac{\frac{1}{25\Omega}}{\frac{1}{50\Omega} + \frac{1}{100\Omega} + \frac{1}{25\Omega}} \quad 7\text{mA} = \frac{4}{7} 7\text{mA} = 4\text{mA}$$

d. Determine the value of I_4 .

e. Determine the value of I_5 .

EE/EET 2240
Homework Problem #008

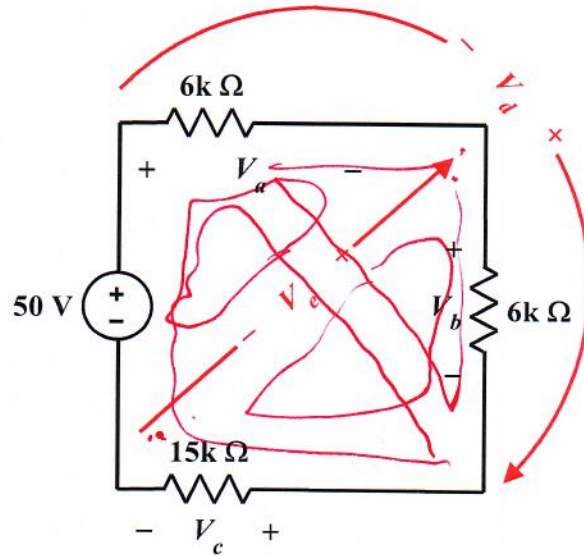

$$V_e = V_b + V_c$$

$$V_e = -V_a + 50$$

- a. Use the voltage divider equation to determine V_a .

$$V_a = \frac{6k\Omega}{6k\Omega + 6k\Omega + 15k\Omega} \cdot 50V = \frac{2}{9} \cdot 50V = \frac{100}{9}V$$

- b. Use the voltage divider equation to determine V_b .


- c. Use the voltage divider equation to determine V_c .

- d. Determine the value of V_d .

- e. Determine the value of V_e .

$$V_e = -\frac{100}{9}V + 50V = \frac{350}{9}V$$

Nodal Analysis

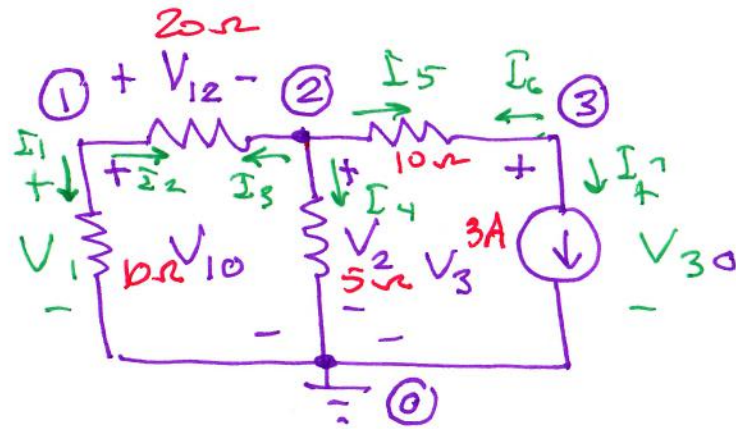

Write a KCL equation for each node other than the reference node.

$$I_1 + I_2 = 0 \quad (\text{KCL})$$

$$I_3 + I_4 + I_5 = 0 \quad (\text{KCL})$$


$$I_6 + I_7 = 0 \quad (\text{KCL})$$

$$\text{Eq. 1: } \frac{V_1}{10\Omega} + \frac{V_1 - V_2}{20\Omega} = 0$$

$$\text{Eq. 2: } \frac{V_2 - V_1}{20\Omega} + \frac{V_2}{5\Omega} + \frac{V_2 - V_3}{10\Omega} = 0$$

$$\text{Eq. 3: } \frac{V_3 - V_2}{10\Omega} + 3 = 0$$


$$\begin{array}{l}
 \text{Eq. 1} \\
 \text{Eq. 2} \\
 \text{Eq. 3}
 \end{array}
 \begin{array}{c}
 V_1 \quad V_2 \quad V_3 \\
 \left[\begin{array}{ccc|ccc}
 3/20 & -1/20 & 0 & V_1 & & \\
 \hline
 -1/20 & 7/20 & -1/10 & V_2 & & \\
 \hline
 0 & -1/10 & 1/10 & V_3 & & \\
 \hline
 & & & & 0 & \\
 & & & & 0 & \\
 & & & & & -3
 \end{array} \right]
 \end{array}
 =
 \begin{array}{c}
 0 \\
 0 \\
 -3
 \end{array}$$

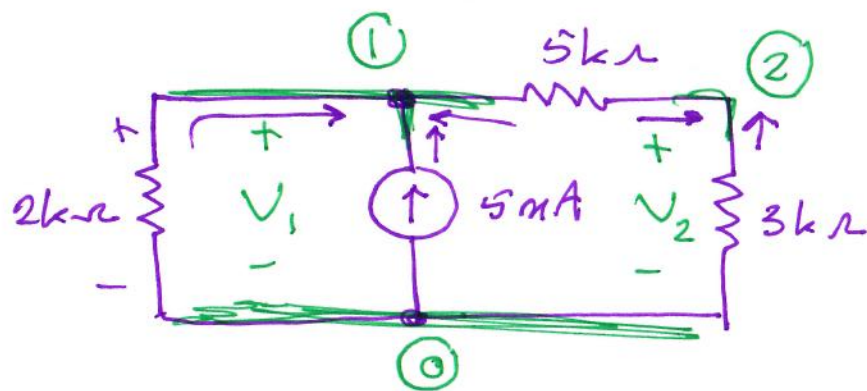

$$-\frac{V_1}{2000\Omega} + \frac{5}{1000} + \frac{V_2 - V_1}{5000} = 0 \quad (\text{KCL at node 1})$$

$$\frac{V_1 - V_2}{5000} - \frac{V_2}{3000} = 0 \quad (\text{KCL at node 2})$$
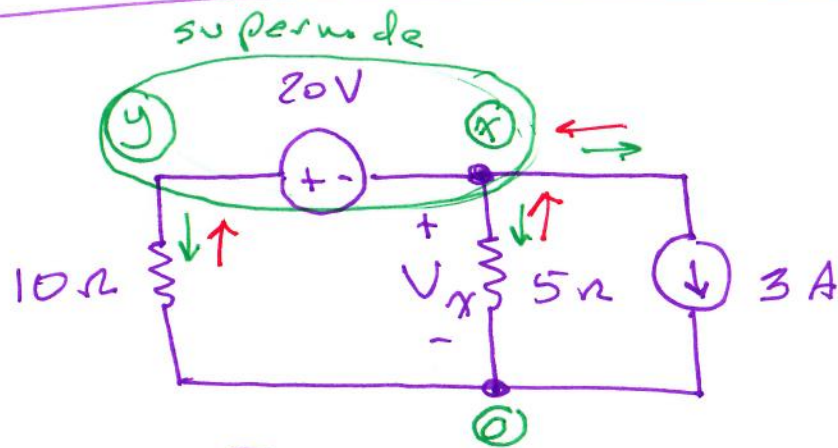
$$\begin{bmatrix} -\frac{7}{10000} & \frac{1}{5000} \\ \frac{1}{5000} & -\frac{2}{15000} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\frac{5}{1000} \\ 0 \end{bmatrix}$$




Find V_x using nodal analysis.

$$V_y - V_x = 20 \quad (\text{constraint equation})$$

$$\frac{V_y}{10} + \frac{V_x}{5} + 3 = 0 \quad (\text{KCL for the Supernode})$$
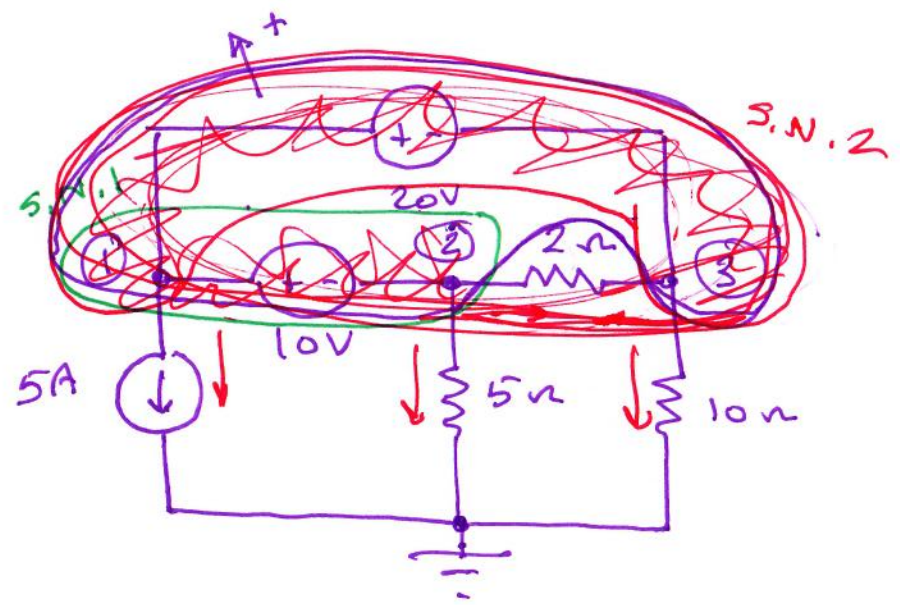
$$+ \left(-\frac{V_y}{10} \right) + \left(-\frac{V_x}{5} \right) - 3 = 0$$




$$V_1 - V_2 = 10 \quad (\text{constraint})$$

$$V_1 - V_3 = 20 \quad (\text{constraint})$$

$$5 + \frac{V_2}{5} + \frac{V_3}{10} = 0 \quad (\text{KCL for supernode})$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 1/5 & 1/10 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 20 \\ -5 \end{bmatrix}$$

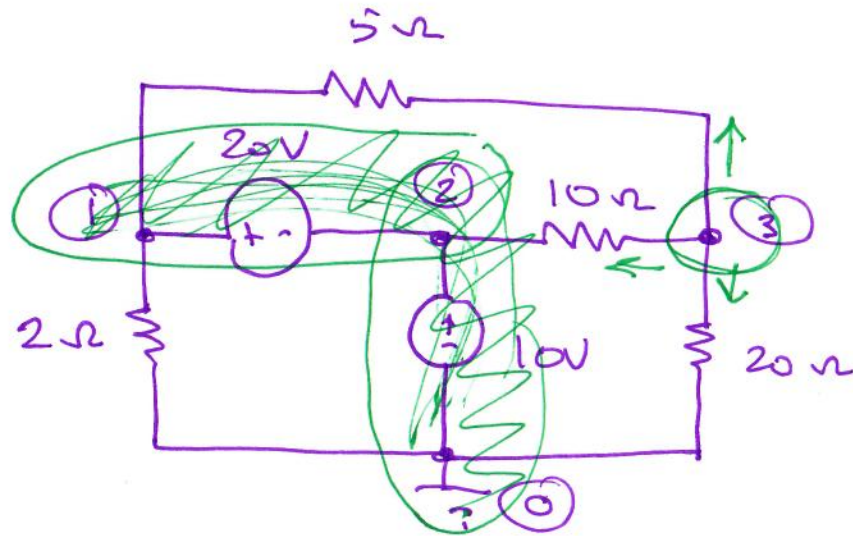Never write a KCL equation for the ref node
or any supernode involving the ref. node.



$$V_1 - V_2 = 20 \quad (\text{constraint})$$

$$V_2 = 10 \quad (\text{constraint})$$

$$\frac{V_3 - V_1}{5\Omega} + \frac{V_3 - V_2}{10\Omega} + \frac{V_3}{20\Omega} = 0 \quad (\text{KCL at node 3})$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & 0 \\ -1/5 & -1/10 & 7/20 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 10 \\ 0 \end{bmatrix}$$