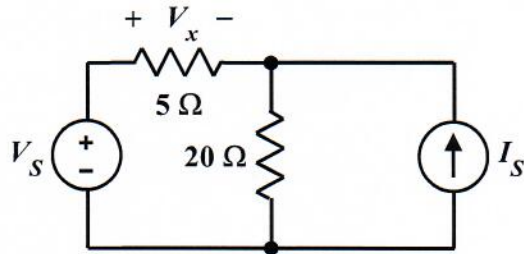





EE/EET 2240
Homework Problem #020



The voltage V_x can be described by the equation

$$V_x = K_1 I_S + K_2 V_S$$

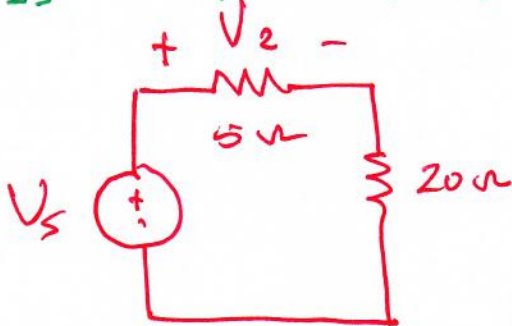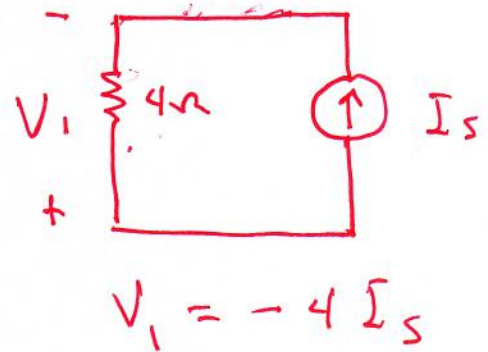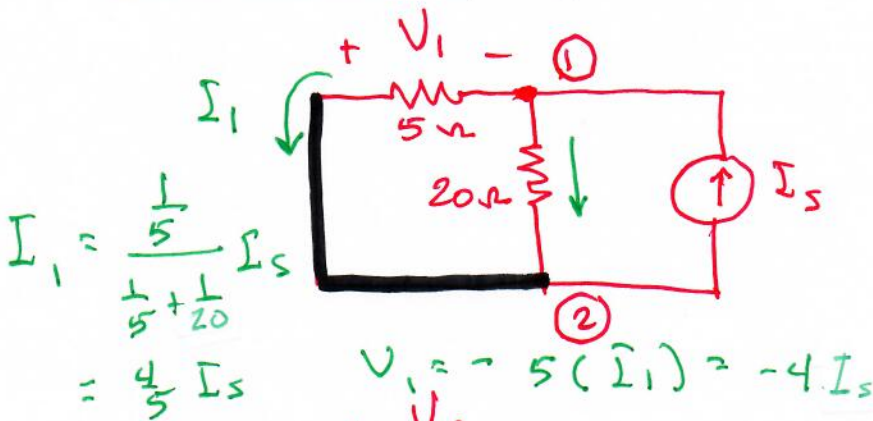where I_S and V_S are the values of the two independent sources. Determine the numerical value of each of the coefficients, K_1 and K_2 .




$$V_2 = \frac{5}{25} V_S = \frac{1}{5} V_S$$


$$V_x = V_1 + V_2 = -4 I_S + \frac{1}{5} V_S$$

$$K_1 = -4, \quad K_2 = \frac{1}{5}$$

EE/EET 2240
Homework Problem #021

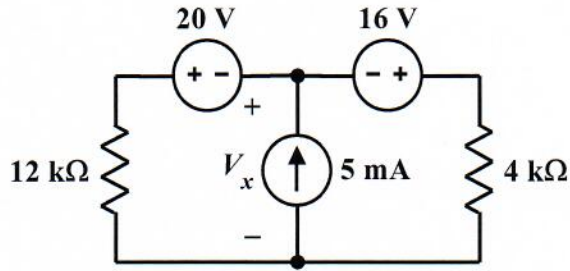


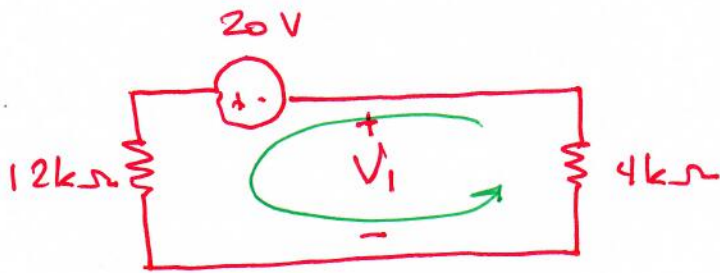Use the superposition method to determine the value of V_x .





$$V_1 = + \frac{4k\Omega}{12k\Omega + 4k\Omega} \cdot 20V$$

$$= -5V$$

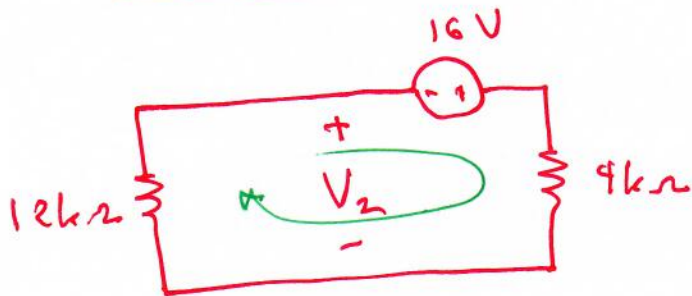

$$V_2 = - \frac{12k\Omega}{12k\Omega + 4k\Omega} \cdot 16V$$


$$= -12V$$

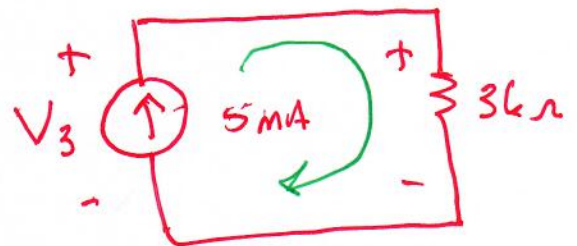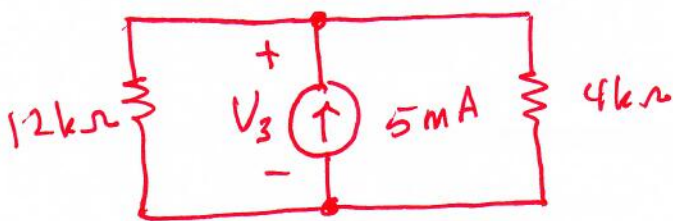

$$V_3 = (3k\Omega)(5mA)$$

$$= 15V$$
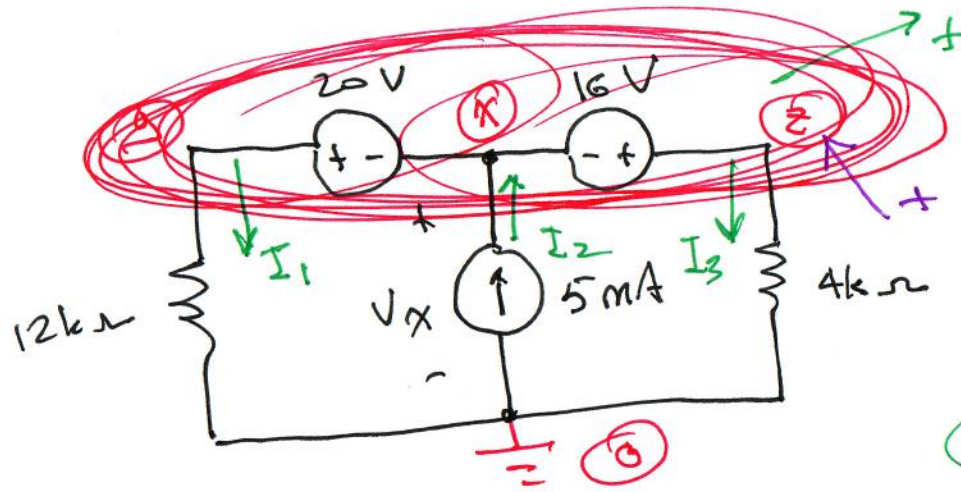
$$V_x = V_1 + V_2 + V_3 = -5 - 12 + 15 = -2V$$



$$\boxed{1} \quad V_y - V_x = 20$$

$$\boxed{2} \quad V_z - V_x = 16$$

$$\frac{V_y}{12k\Omega} + \frac{V_z}{4k\Omega} - \frac{5}{1000} = 0$$

$$\boxed{3} \quad \Rightarrow \quad V_y + 3V_z - 60 = 0$$

$$\boxed{1} - \boxed{2} \quad \Rightarrow \quad V_y - V_z = 4$$

$$\boxed{3} \quad \Rightarrow \quad V_z + 3V_z = 60$$

$$4V_z = 60 \quad \Rightarrow \quad V_z = 15V$$

$$V_x = V_z - 16 = 15 - 16 = -1V$$


$$\hat{I}_1 + \hat{I}_3 - \hat{I}_2 = 0$$

$$\hat{I}_2 = \hat{I}_1 + \hat{I}_3$$

$$\hat{I}_2 - \hat{I}_1 - \hat{I}_3 = 0$$

Homework Problem #019

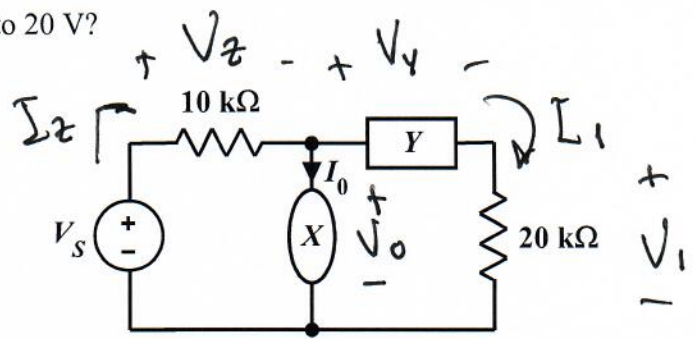X and Y are linear components. If $I_0 = 15 \text{ mA}$ when $V_s = 60 \text{ V}$, what will be the new value of I_0 if V_s is decreased to 20 V ?



$$I_0 = K V_s$$

$$15 \text{ mA} = K (60 \text{ V})$$

$$K = \frac{15 \text{ mA}}{60} = .25 \text{ mA/V}$$

$$V_0 = K_1 V_s$$

$$I_1 = K_2 V_s$$

$$V_1 = K_3 V_s$$

$$V_y = K_4 V_s$$


$$V_z = K_5 V_s$$


$$I_2 = K_6 V_s$$

$$I_0' = K (20 \text{ V}) = 5 \text{ mA}$$

Thévenin's Theorem

Norton's Theorem

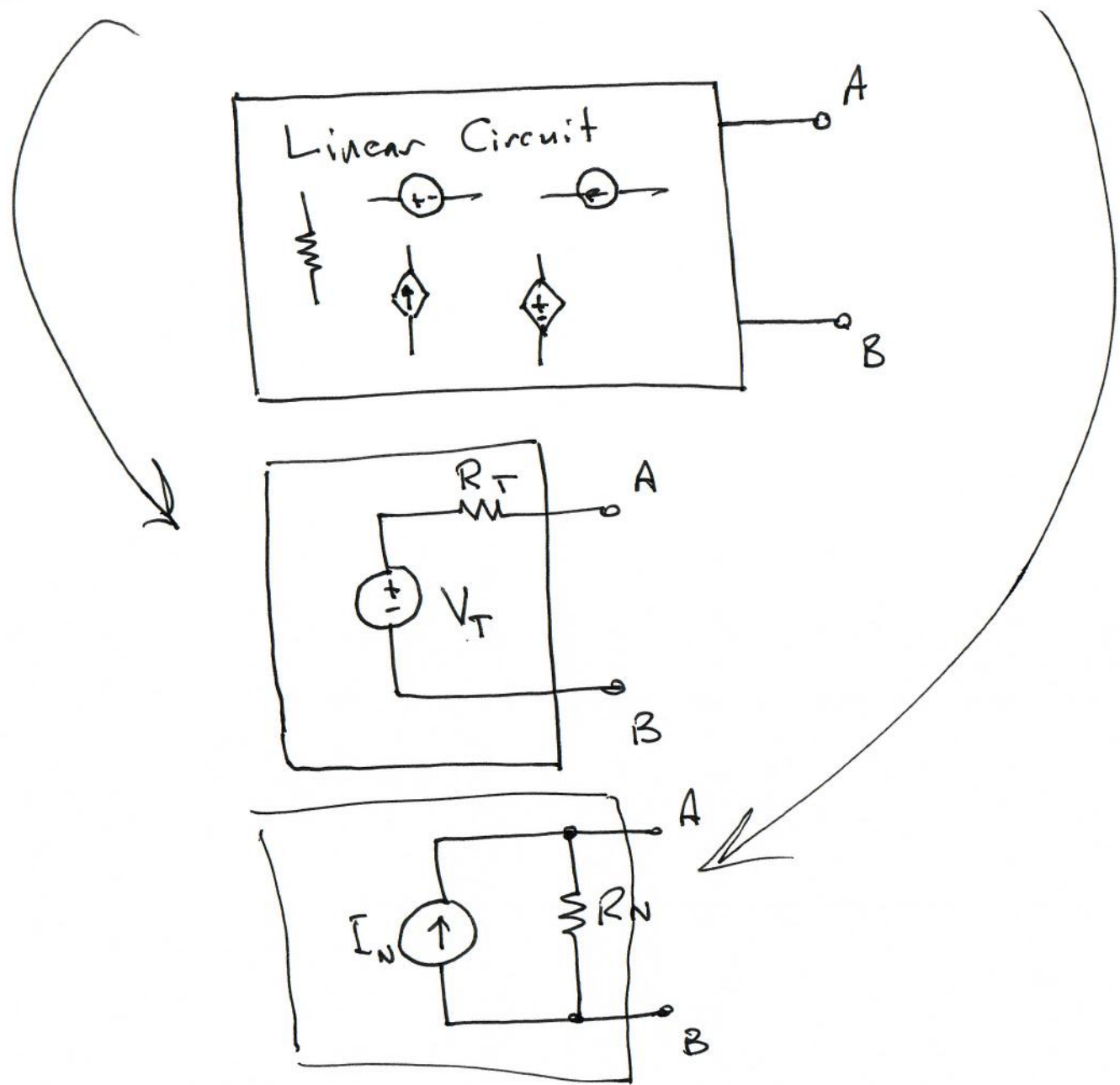


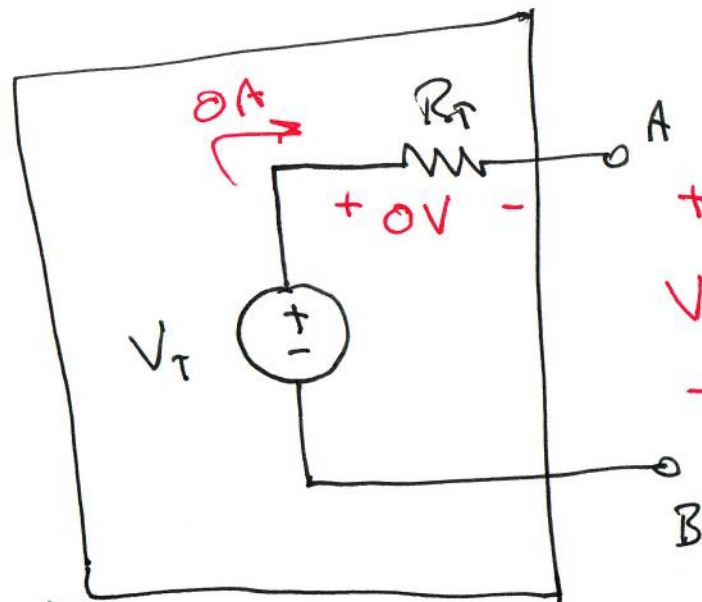

$$V_{oc} = V_T$$

Measure or calculate


Thevenin Equivalent

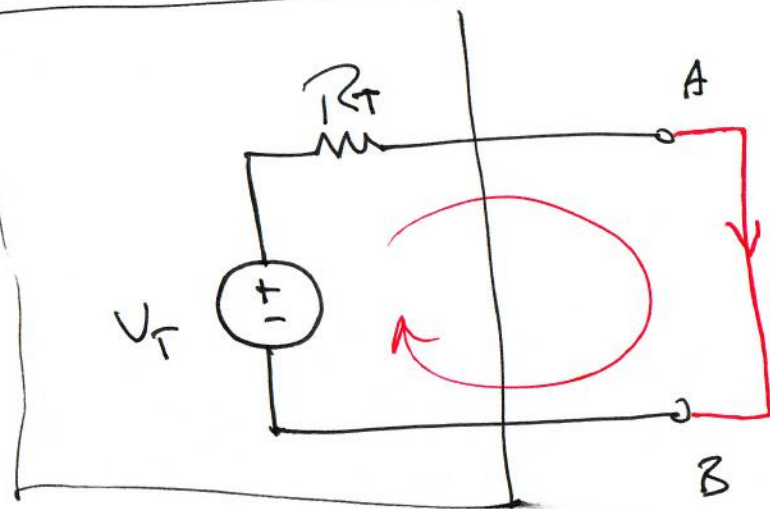


$$I_{sc} = \frac{V_T}{R_T}$$

Measure or calculate


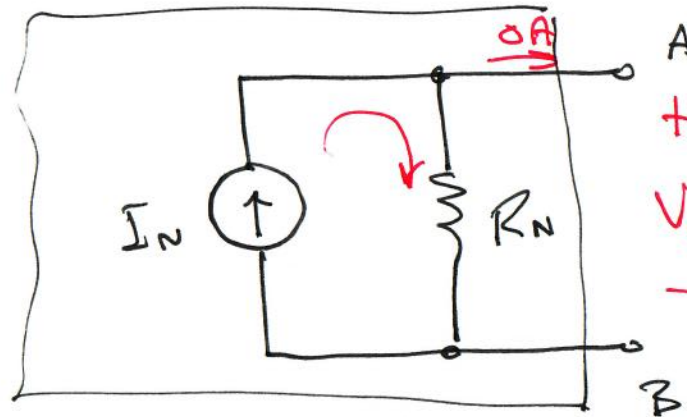
$$R_T = \frac{V_T}{I_{sc}} = \frac{V_{oc}}{I_{sc}}$$




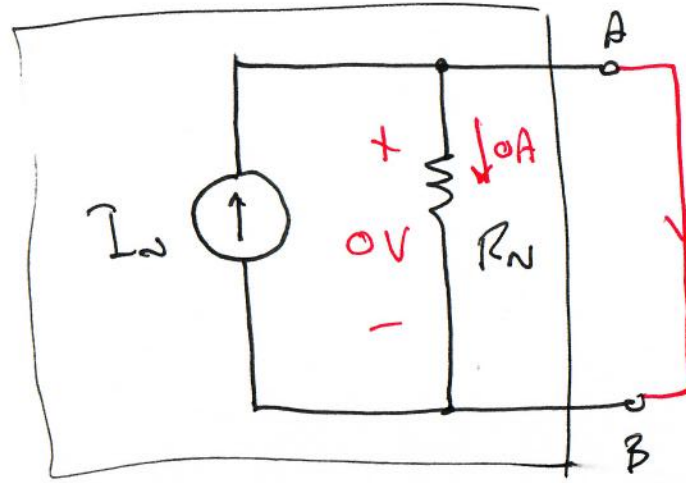
$$V_{oc} = R_N I_N = R_N I_{sc}$$
$$R_N = \frac{V_{oc}}{I_{sc}}$$





$$I_{sc} = I_N$$

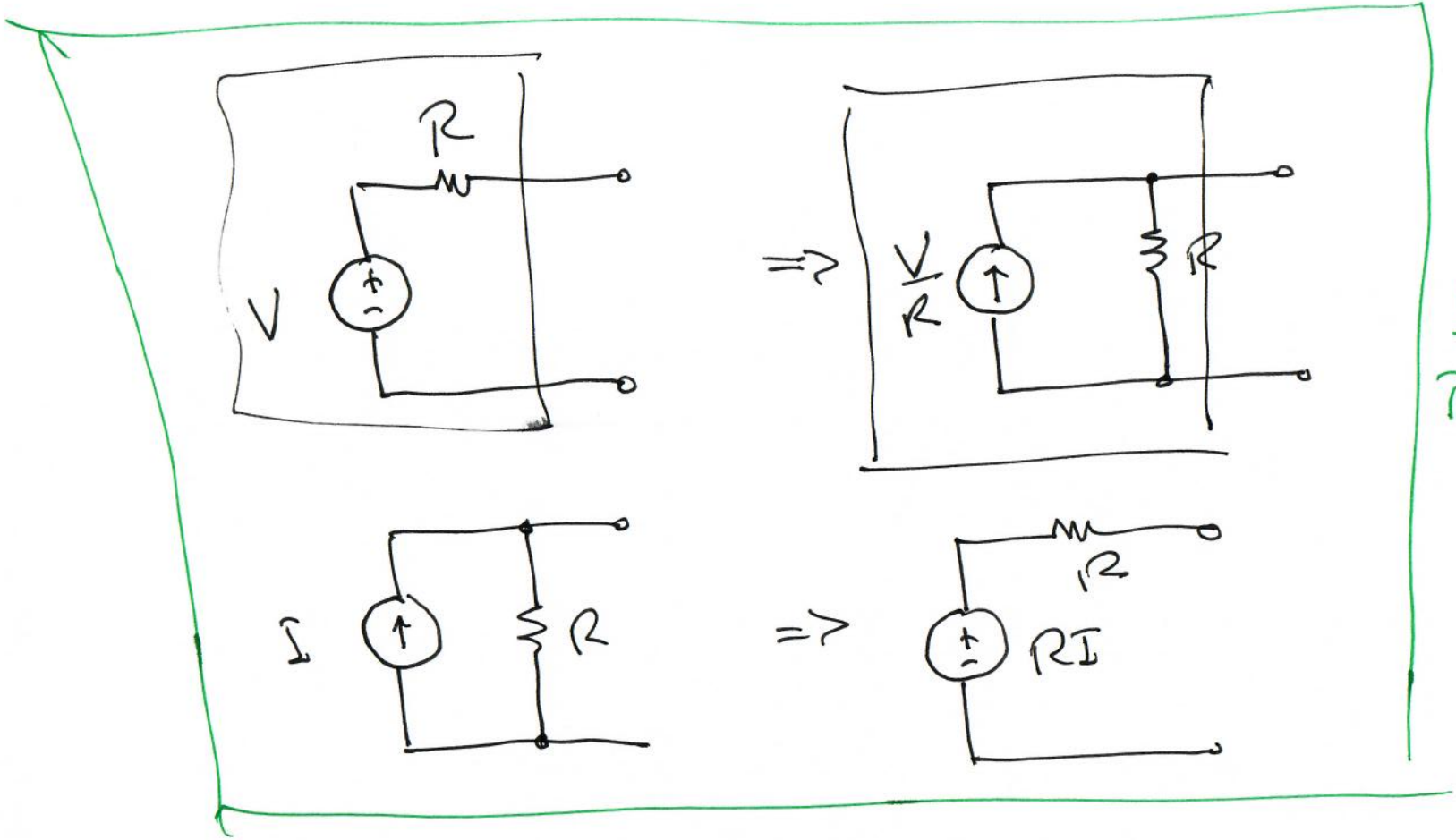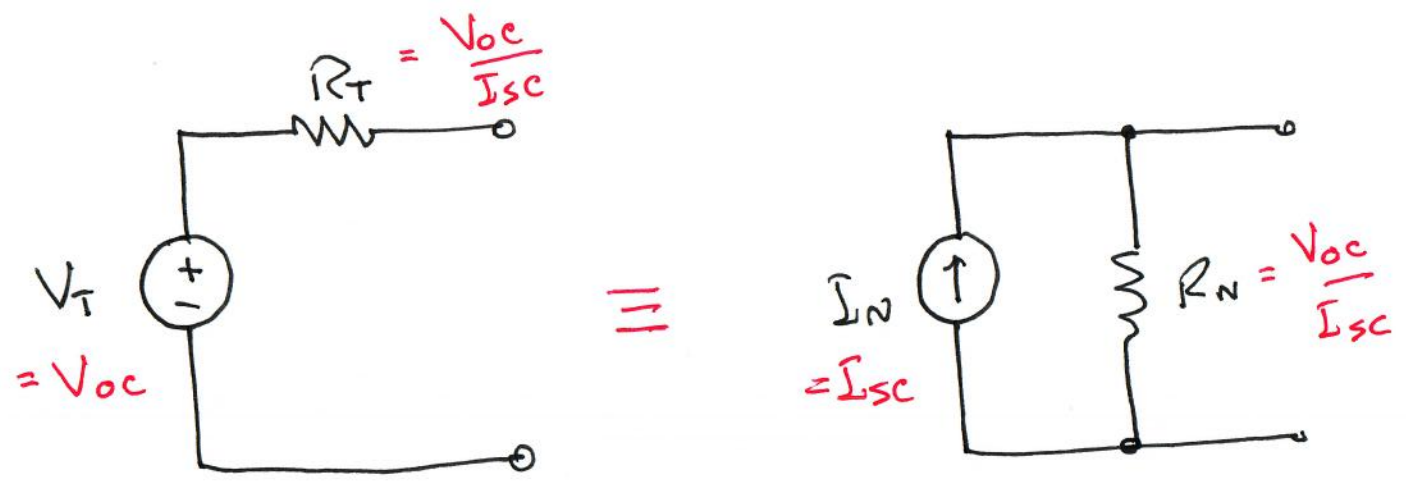

Source Transformation

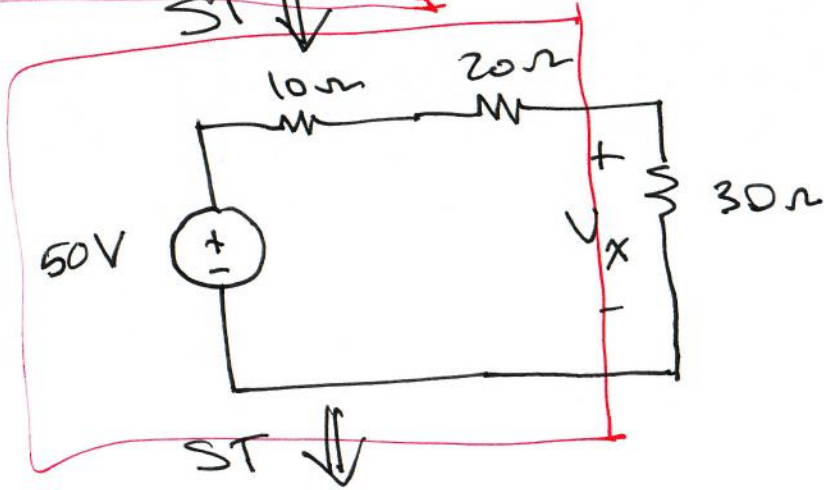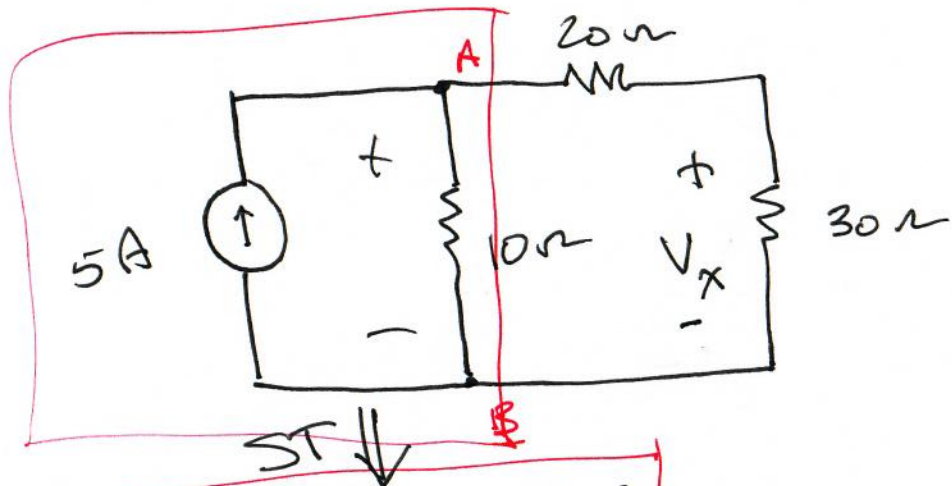

$$V_x = \frac{30}{60} \cdot 50 = 25V$$

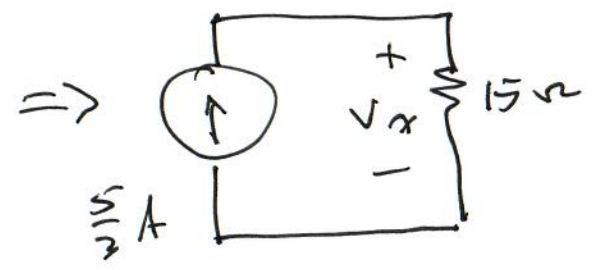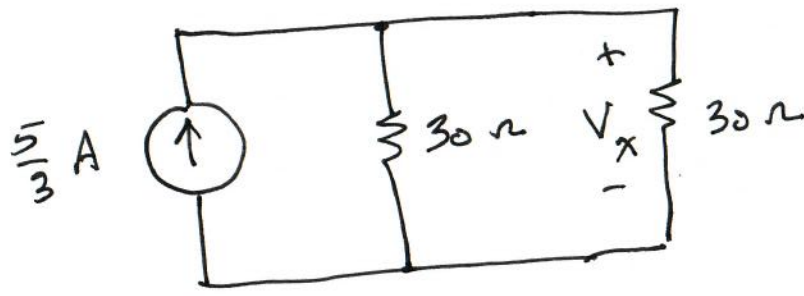

$$V_x = \frac{5}{3} \cdot 15 = 25V$$