

EE 2240  
**Problem #05**

Accurately sketch the waveform for the current through a  $6 \mu\text{F}$  capacitor when the capacitor voltage is as shown.

