

EE 2240  
**Problem #08**

The waveform for the current in a  $1000\ \mu\text{F}$  initially uncharged capacitor is shown. Determine and accurately sketch the waveform for the capacitor's voltage.

