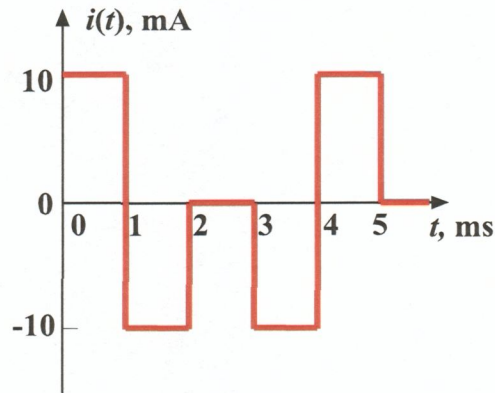


EE 2240
Problem #08

The waveform for the current in a $1000 \mu\text{F}$ initially uncharged capacitor is shown. Determine and accurately sketch the waveform for the capacitor's voltage.



$$v(t) = v(0) + \frac{1}{C} \int_0^t i(t) dt$$

$$= 0 + 10^3 \int_0^t i(t) dt$$

$$= \begin{cases} 0 & : t=0 \\ 0 + 10^3 \int_0^t (10 \times 10^{-3}) dt = 10t \text{ V} & : 0 < t < 1 \text{ ms} \\ 0.01 + 10^3 \int_{1 \text{ ms}}^t (-10 \times 10^{-3}) dt = 0.02 - 10t \text{ V} & : 1 \text{ ms} < t < 2 \text{ ms} \\ 0 & : 2 \text{ ms} < t < 3 \text{ ms} \\ 0 + 10^{-3} \int_{3 \text{ ms}}^t (-10 \times 10^{-3}) dt = 0.03 - 10t \text{ V} & : 3 \text{ ms} < t < 4 \text{ ms} \\ -0.01 + 10^3 \int_{4 \text{ ms}}^t (10 \times 10^{-3}) dt = -0.05 + 10t \text{ V} & : 4 \text{ ms} < t < 5 \text{ ms} \\ 0 & : 5 \text{ ms} < t \end{cases}$$

