

EE 2240
Problem #03

Use PSpice to determine V_x .

