

EE 2240
Problem #06

Node and component labels have been pre-assigned in the circuit shown. Use PSpice to determine the value of V_x .

