

EE 2240  
**Problem #01**

Determine the value of  $V_o$ .

