

EE 2240
Problem #02

Determine the value of V_o .

