

EE 2240
Problem #03

The current in a 10 mH inductor is given by the waveform shown. Find, and accurately sketch, the waveform for the voltage across that inductor.

