

EE 2240
Problem #04

The waveform for the voltage across a $20\ \mu\text{H}$ inductor is shown. Determine, and accurately sketch, the waveform for the inductor current if $v(t) = 0$ for $t < 0$.

