

EE 2240
Problem #05

Given $I_1 = -20$ mA, $I_2 = -12$ mA, and $I_3 = 50$ mA, find I_4 , I_5 , and I_6 .

