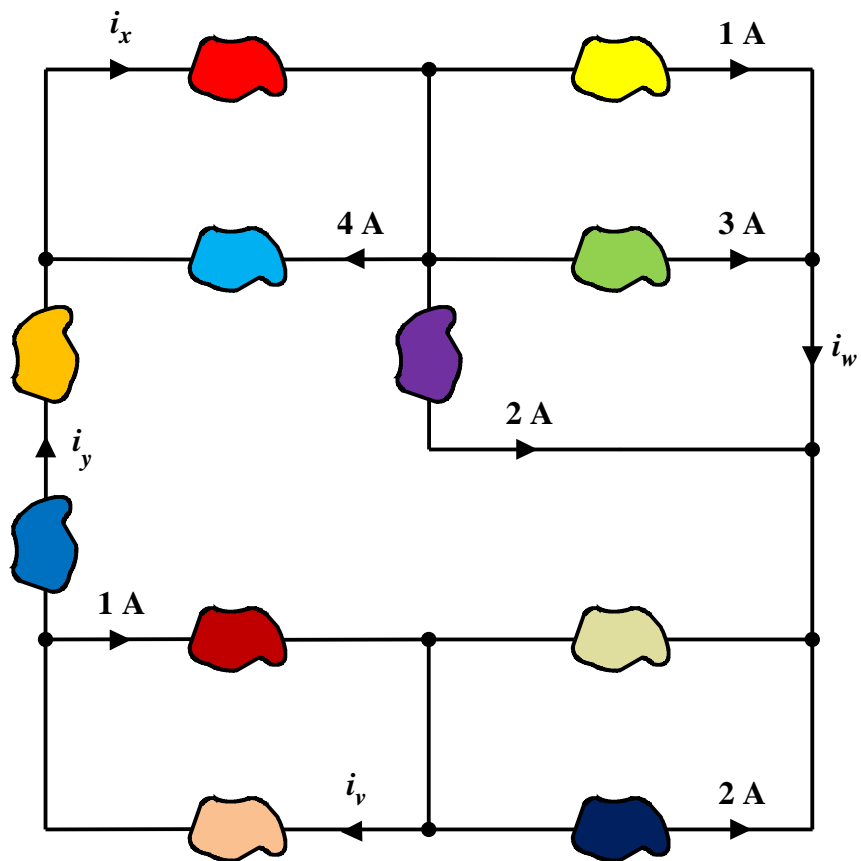


EE 2240  
**Problem #09**

Given the following circuit:



- Find  $i_v$ .
- Find  $i_w$ .
- Find  $i_x$ .
- Find  $i_y$ .