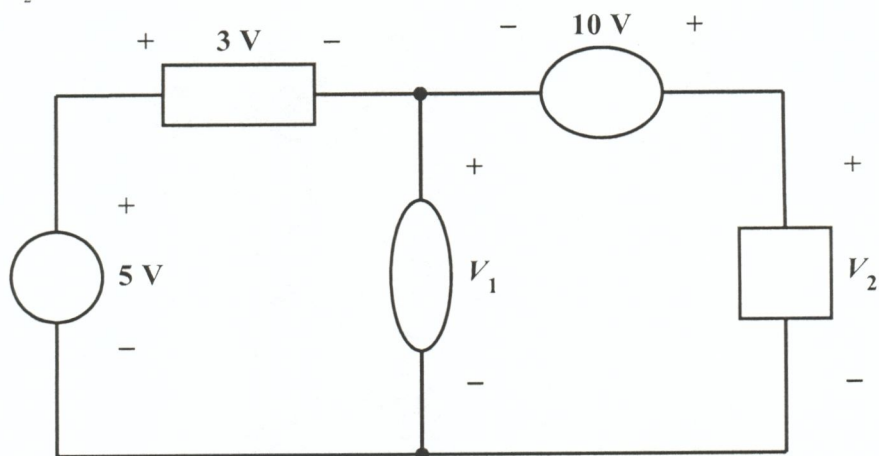


EE 2240  
Problem #08

Find  $V_1$  and  $V_2$ .



$$V_1 = -3V + 5V = 2V$$

$$V_2 = 10V - 3V + 5V = 12V$$