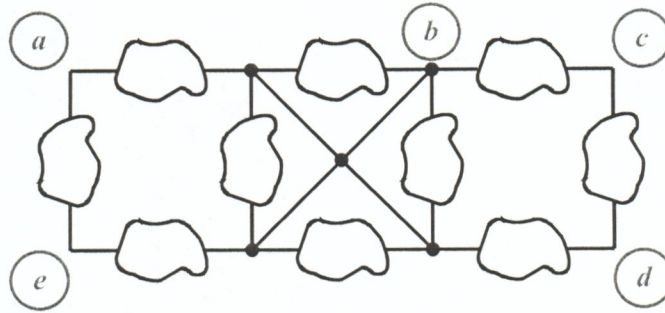


EE 2240
Problem #11

Several of the nodes in the circuit shown below are labeled.



If $V_{ab} = 10\text{ V}$, $V_{ac} = 5\text{ V}$, $V_{ae} = 1\text{ V}$ and $V_{db} = 3\text{ V}$:

a. Determine V_{ad} .

$$V_{ad} = V_{ab} + V_{bd} = V_{ab} - V_{db} = 10\text{V} - 3\text{V} = 7\text{V}$$

b. Determine V_{dc} .

$$\begin{aligned} V_{dc} &= V_{db} + V_{ba} + V_{ac} = V_{db} - V_{ab} + V_{ac} \\ &= 3\text{V} - 10\text{V} + 5\text{V} = -2\text{V} \end{aligned}$$

c. Determine V_{bd} .

$$V_{bd} = -V_{db} = -3\text{V}$$

d. Determine V_{ce} .

$$V_{ce} = V_{ca} + V_{ae} = -V_{ac} + V_{ae} = -5\text{V} + 1\text{V} = -4\text{V}$$

e. Determine V_{de} .

$$\begin{aligned} V_{de} &= V_{db} + V_{ba} + V_{ae} \\ &= V_{db} - V_{ab} + V_{ae} \\ &= 3\text{V} - 10\text{V} + 1\text{V} \\ &= -6\text{V} \end{aligned}$$