

EE 2240
Problem #01

Use linearity and proportionality, with an initial assumption that $V_o = 40\text{ V}$, to find V_o . Show the details of your work.

