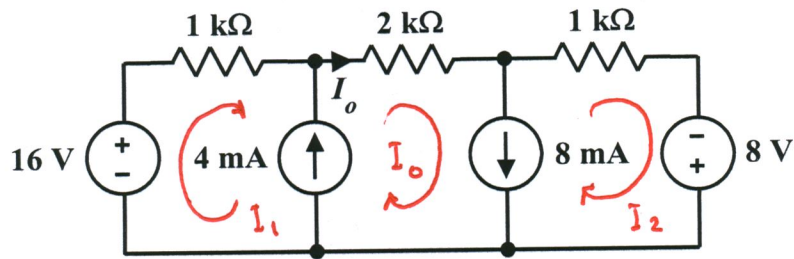


EE 2240
Problem #09



- a. How many equations are necessary to analyze this circuit by the mesh analysis method?

3

Use the method discussed in class to:

- b. Develop the mesh equations describing the circuit.

$$I_o - I_1 = 4 \text{ mA}$$

$$I_o - I_2 = 8 \text{ mA}$$

$$-16 \text{ V} + (1 \text{ k}\Omega) I_1 + (2 \text{ k}\Omega) I_o + (1 \text{ k}\Omega) I_2 - 8 \text{ V} = 0$$

- c. Write the mesh equations in the matrix form discussed in class.

$$\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 2000 & 1000 & 1000 \end{bmatrix} \begin{bmatrix} I_o \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.004 \\ 0.008 \\ 24 \end{bmatrix}$$

- d. Solve the mesh equations to determine the value of I_o .

$$I_o = 9 \text{ mA}$$