

EE 2240
Problem #01

Use Norton's Theorem to find I_o .

