

EE 2240  
**Problem #01**

Find the current  $I$  and the power supplied by the source.

