

EE 2240  
**Problem #02**

Find the voltage across the current source and the power absorbed by the resistor.

