

EE 2240
Problem #06

Calculate the value of V_{out} .

