

EE 2240
Problem #01

Determine whether each component *absorbs* or *delivers* power.

