

EE 2240  
**Problem #02**

Does component  $Z$  *deliver* power or *absorb* power? How much?

