

EE 2240  
Problem #03

Does component  $Z$  deliver power or absorb power? How much?

