

EE 2240
Problem #04

Assuming each is a passive component (i.e., absorbs power), determine the total power absorbed by components 1, 2 and 3.

