

EE 2240  
**Problem #01**

The capacitor is initially charged such that  $v_C(0) = 12 \text{ V}$ . Determine and solve the differential equation for  $v_C(t)$  for all  $t \geq 0$ .

