

EE 2240
Problem #02

Consider the RC circuit shown below, where $v_C(0) = 8 \text{ V}$. The accompanying plot is alleged to show the transient response of the circuit. A point on the curve has been labeled, indicating a time and the corresponding capacitor voltage. Determine whether or not the plot is a true representation of the capacitor voltage in this circuit.

