

EE 2240
Problem #05

Given $v_C(0) = 10 \text{ V}$, determine $v_C(\infty)$ and $v_C(t)$ for $t \geq 0$.

