

EE 2240  
**Problem #07**

The circuit has reached the DC steady state prior to  $t = 0$ . Find  $i_o(t)$  for  $t \geq 0$ .

