

EE 2240  
**Problem #02**

For the underdamped circuit shown, determine the current  $i_L(t)$  if the initial conditions on the storage elements are  $i_L(0) = 1$  A and  $v_C(0) = 10$  V.

