

EE 2240
Problem #03

Find $v_C(t)$ for $t \geq 0$ if $v_C(0) = 20$ V and $i_L(0) = 500$ mA.

