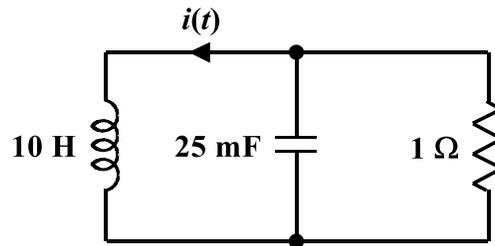


EE 2240
Problem #09

At $t = 0$, no energy is stored in the circuit shown below.



Find $i(t)$ for $t \geq 0$.