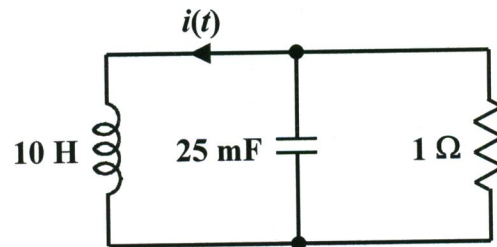


EE 2240  
Problem #09

At  $t = 0$ , no energy is stored in the circuit shown below.



Find  $i(t)$  for  $t \geq 0$ .

If no energy is stored at  $t = 0$ ,  
then  $i(t) = 0$  for  $t \geq 0$