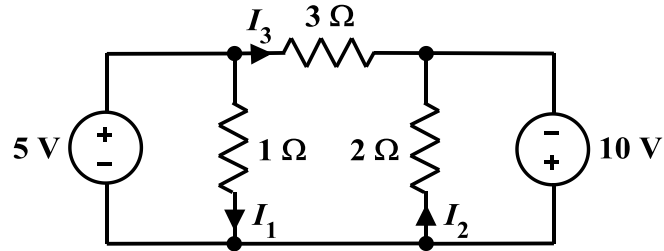


EE 2240
Problem #02



- Determine the value of I_1 .
- Determine the value of I_2 .
- Determine the value of I_3 .
- How much power is delivered by the 5 V independent voltage source?
- How much power is delivered by the 10 V independent voltage source?