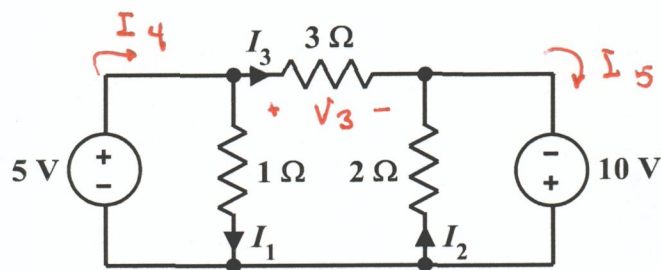


EE 2240  
Problem #02



- a. Determine the value of  $I_1$ .

$$I_1 = \frac{5V}{1\Omega} = 5A$$

- b. Determine the value of  $I_2$ .

$$I_2 = \frac{10V}{2\Omega} = 5A$$

- c. Determine the value of  $I_3$ .

$$V_3 = 5 + 10 = 15V$$

$$\therefore I_3 = \frac{V_3}{3\Omega} = 5A$$

- d. How much power is delivered by the 5 V independent voltage source?

$$I_4 = I_1 + I_3 = 5 + 5 = 10A$$

$$\therefore P = (5V)I_4 = 50W$$

- e. How much power is delivered by the 10 V independent voltage source?

$$I_5 = I_2 + I_3 = 5 + 5 = 10A$$

$$\therefore P = (10V)(10A) = 100W$$