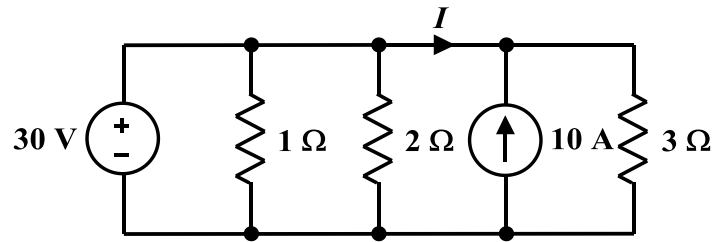


EE 2240
Problem #04



- Determine the power absorbed by the 1 Ω resistor.
- Determine the value of I .
- Determine the power absorbed by the 3 Ω resistor.
- How much power is delivered by the 30 V independent voltage source?
- How much power is delivered by the 10 A independent current source?