

Problem #01

Use source transformations to reduce the circuit shown below to its simplest possible equivalent with respect to terminals A-B.

