
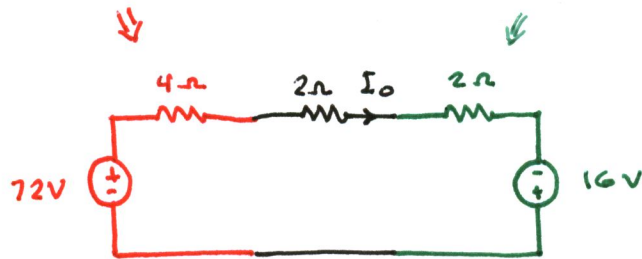
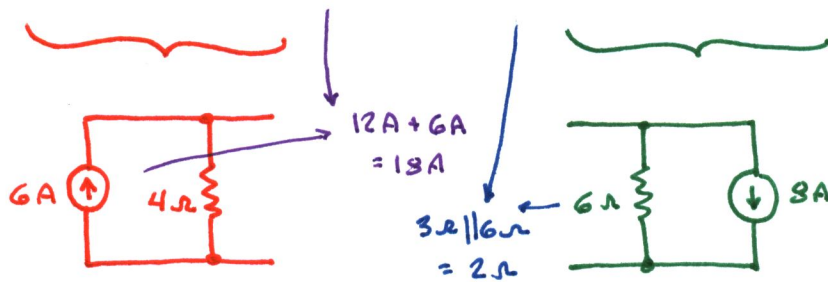


EE 2240
Problem #03

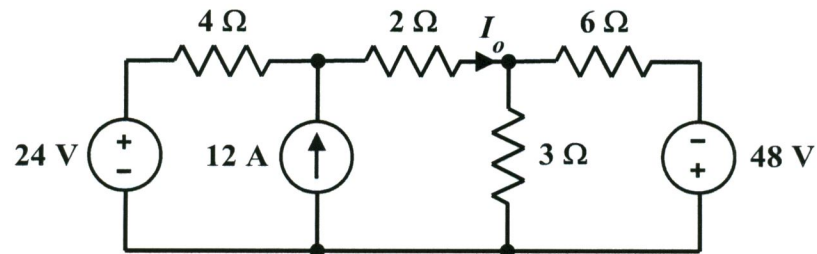Use a sequence of source transformations to find I_o .



$$I_o = \frac{72V + 16V}{4\Omega + 2\Omega + 2\Omega} = 11A$$