

EE 2240
Problem #02

Determine the capacitance of the unknown capacitor, C_x , and the amount of energy stored in it.

